

DIODE CLIPPING CIRCUITS

Aim: To design and test diode clipping circuits for peak clipping and peak detection.

Components required:

- Power Supply
- Diodes IN4007or BY127
- Resistors


Procedure:

- Make the Connections as shown in the circuit diagram
- Apply sinusoidal input V_i of 1 KHz and of amplitude 8V P-P to the circuit.
- Observe the output signal in the CRO and verify it with given waveforms.
- Apply V_i and V_o to the X and Y channel of CRO and observe the transfer characteristic waveform and verify it.

I) Positive Clipping


Circuit: Circuit


Diagram:

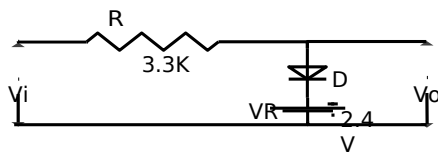

8Vp-p

Waveforms:

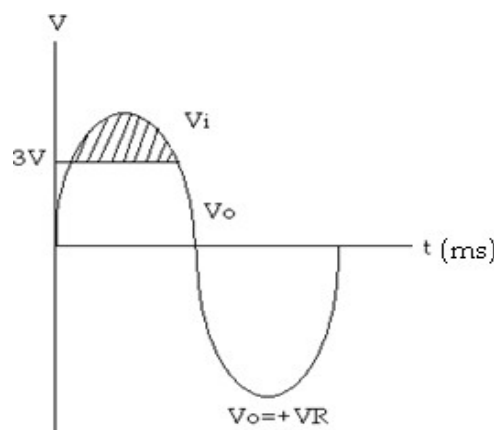

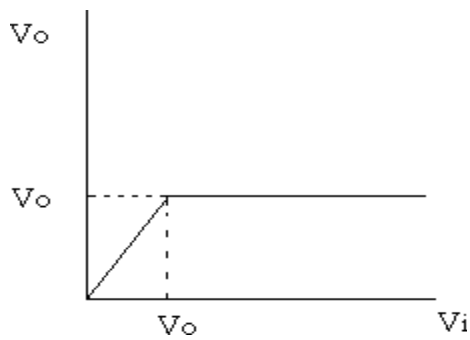Transfer Characteristics:**To find the value of R:**

Given: $R_f = 100\Omega$, $R_r = 100K\Omega$

R_f - Diode forward
resistance R_r - Diode
reverse resistance

$$R = \sqrt{R_f R_r} = \sqrt{100 \times 100 \times 10^3} = 3.16K\Omega$$

Choose R as 10 K Ω

Let the output voltage be clipped at

$$+3V \quad V_{omax} = 3V$$

\therefore

From the circuit diagram,

$$V_{omax} = V_r + V_{ref}$$

Where V_r is the diode drop =

$$\therefore 0.6V \quad V_{ref} = V_{omax} - V_r$$


$$= 3 - 0.7$$

$$\mathbf{V_{ref} = 2.3 V}$$


II) Negative Clipping

Circuit: Circuit


Diagram:

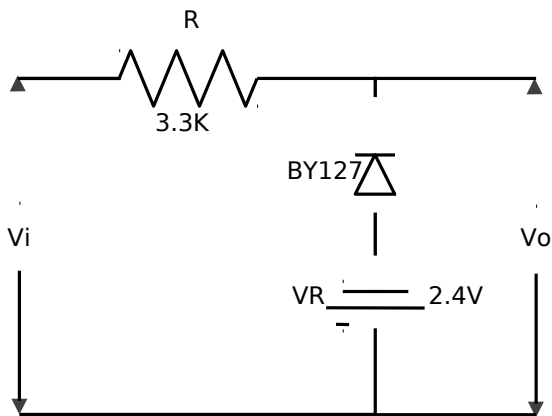

Waveforms:

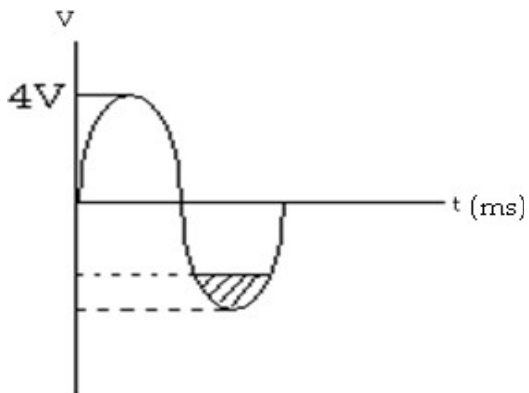

Transfer Characteristics:

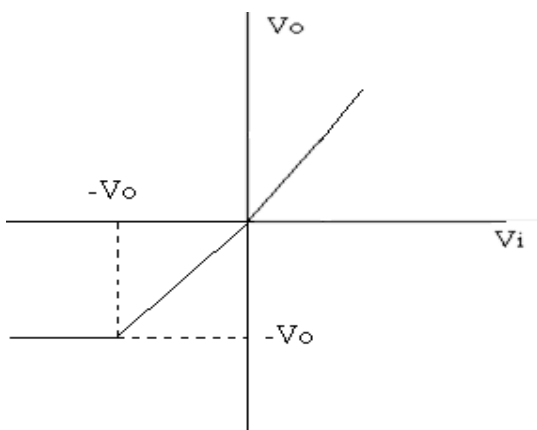

Let the output voltage be clipped at

$$-3V \quad V_{omin} = -3V$$

$$V_{omin} = -V_r + V_{ref}$$

$$V_{\text{ref}} = V_{\text{omin}} + V_r = -3 + 0.7$$

$$\mathbf{V_{\text{ref}} = -2.3V}$$

CLAMPING CIRCUITS

Aim: Design and test positive and negative clamping circuit for a given reference voltage.

Components required:

- Power Supply
- CRO
- Signal Generator
- Diode BY 127
- Resistors
- Capacitor

Design:

R_f - Diode forward resistance =

100Ω R_r - Diode Reverse

resistance = 1M Ω $R = \sqrt{R_f R_r} =$

10KΩ

$RC \gg T$ let $T = 1\text{ms}$

f(1KHz) Let $RC =$

10T

$RC = 10\text{ms}$

$C = 1\mu\text{F}$


$R =$

10KΩ

I) Positive Clamping

Circuits: Circuit


Diagram:

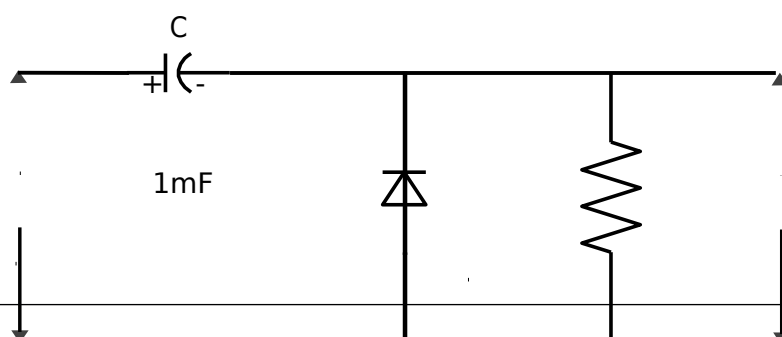


D BY127 R 10K Vo

8Vp-p Vi

Waveforms:

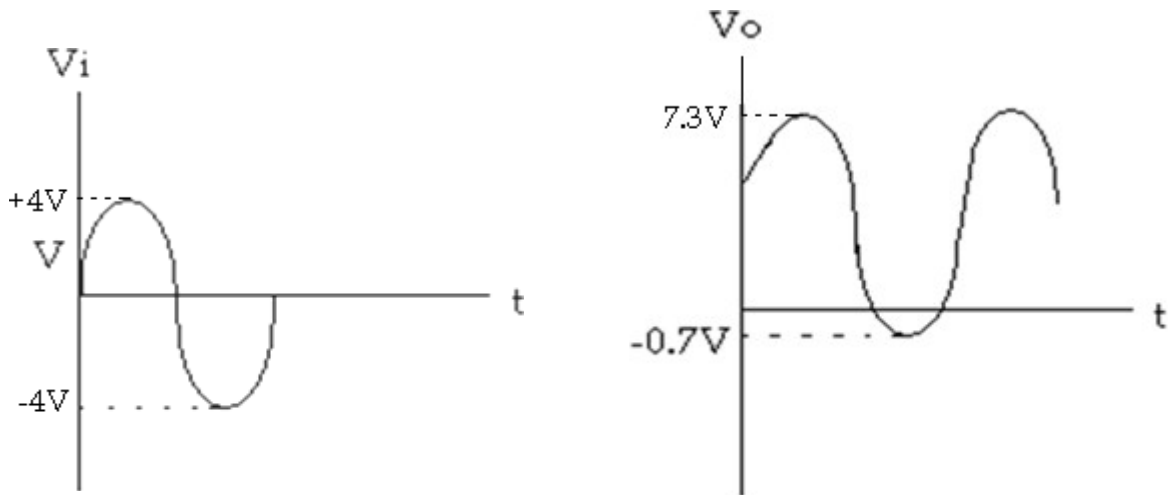

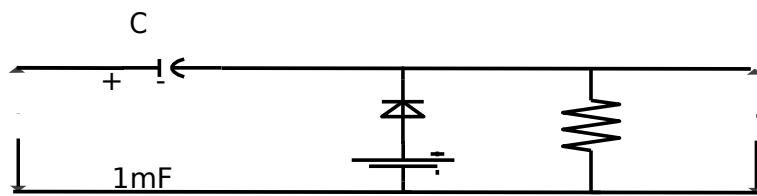II) Design a Clamping Circuit to Clamp Negative Peak at +3V:




$8V_{p-p}$ V_i

R $10K$ V_o

V_{ref} $3.6V$

Waveforms:

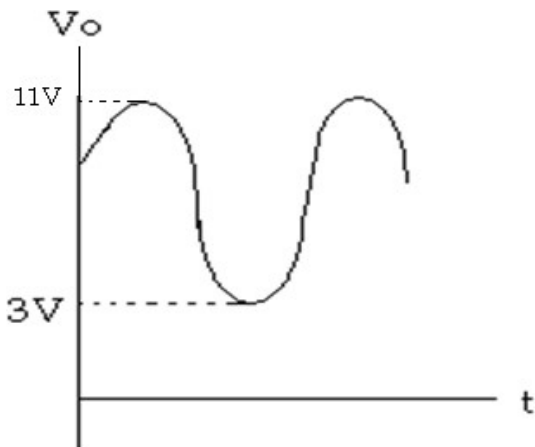

$$V_o = V_{\theta} +$$

$$V_{ref} = 3 = -0.7$$


+ V_{ref}

$V_{\text{ref}} = 3.7$

III) Negative Clamping


Circuit: Circuit

Diagram:

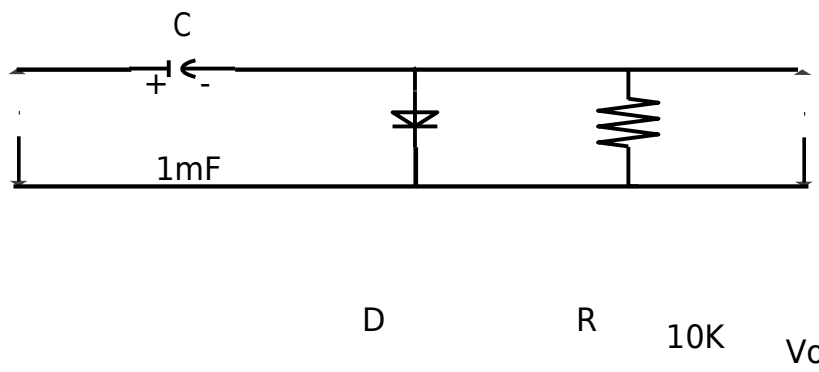

8Vp-p
Vi

Waveforms:

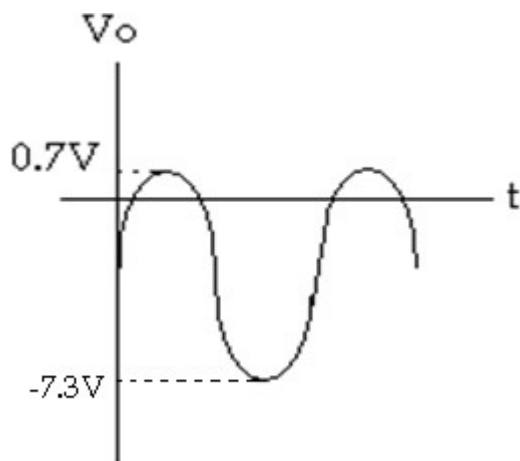

RECTIFIER CIRCUITS

Aim: To design and test Half wave, Full wave, Bridge Rectifier circuits with & without capacitor filter and determine the Ripple factor, Regulation & Efficiency.

Components required:

- Resistors
- Diodes
- 12-0-12V Transformer
- Capacitor

Calculations:

Assume $R_L = 4.7K\Omega$, $C = 220\mu F$

I) Half wave Rectifier:

1. Ripple Factor without Filter (Theoretical) = 1.21

2. Percentage Regulation = $\frac{R_f}{R_L} \times 100$ (R_f = Diode forward resistance)

3. Rectifier Efficiency $\eta = \frac{0.406}{1 + \frac{R_f}{R_L}} \approx 40.6\%$

4. γ Ripple Factor without Filter = $\frac{1}{2\sqrt{3} f R_L C}$ (f = frequency = 50Hz)

II) Full wave Rectifier:

1. Ripple Factor without Filter = 0.48

2. Percentage Regulation = $\frac{R_f}{R_L} \times 100$

3. Rectifier Efficiency $\eta = 81\%$

4. γ Ripple Factor without Filter = $\frac{0.81}{4\sqrt{3} f C R_L}$

III) Bridge Rectifier:

1. Ripple Factor without Filter = 0.48


2. Percentage Regulation = $\frac{R_f}{R_L} \times 100$

3. Rectifier Efficiency $\eta = 81\%$



$$\frac{0.81}{1 + \frac{R_f}{R_L}} =$$

I) Half wave Rectifier without

Filter: Circuit Diagram:

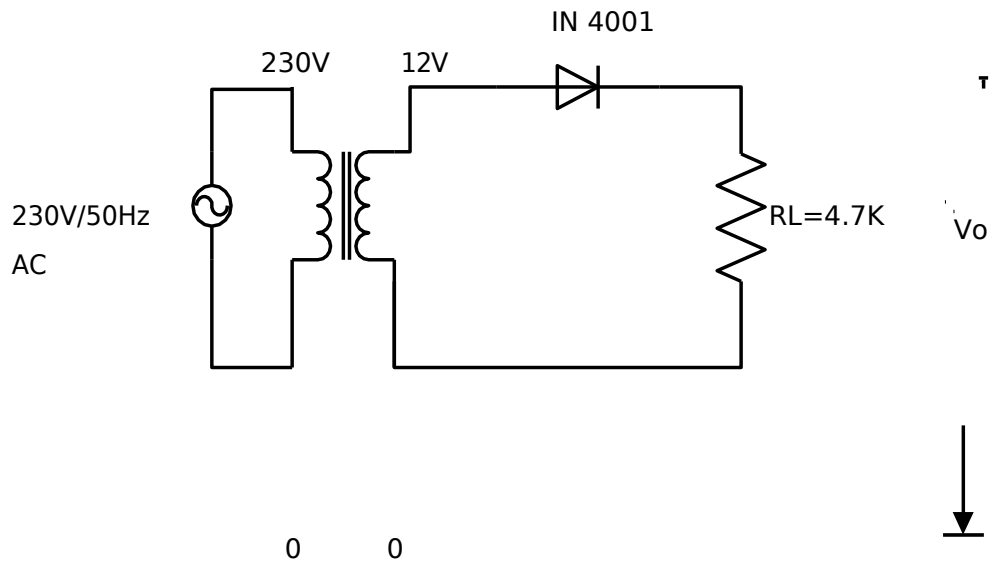

Waveforms:

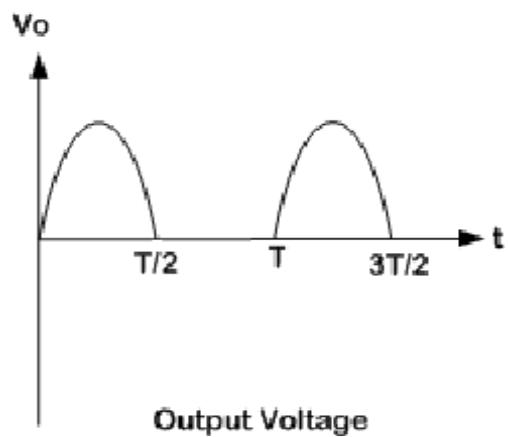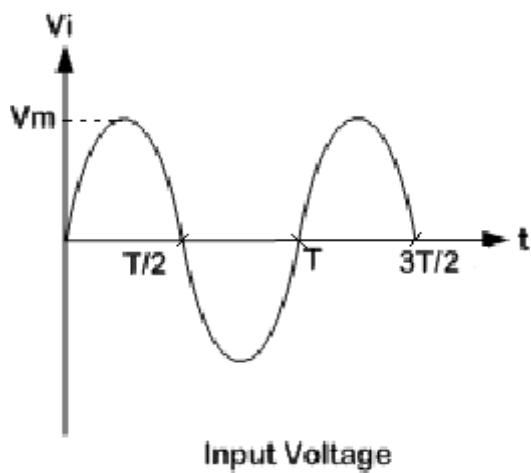

Peak output voltage

$$V_m = V_{dc} = \frac{V_m}{\pi} =$$


$$V_{rms} = \frac{V_m}{2} =$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} =$$


Ripple Factor $\gamma = \frac{V_{ac}}{V_{dc}} =$

Rectifier efficiency $\eta = = \frac{V_{dc(NL)} - V_{dc(FL)}}{\frac{P_{dc(FL)}}{P_{ac}} \frac{V_{dc}^2}{V_{rms}^2}} \times 100 =$ % Regulation =

Half wave Rectifier with Filter:

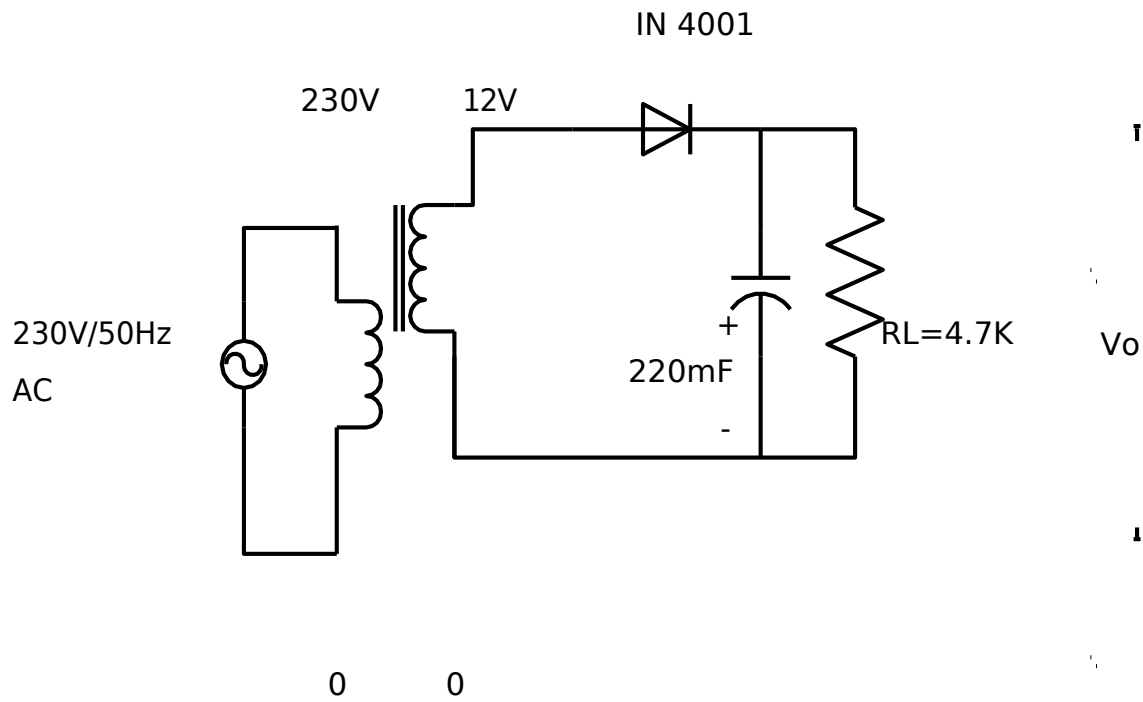

Waveforms:

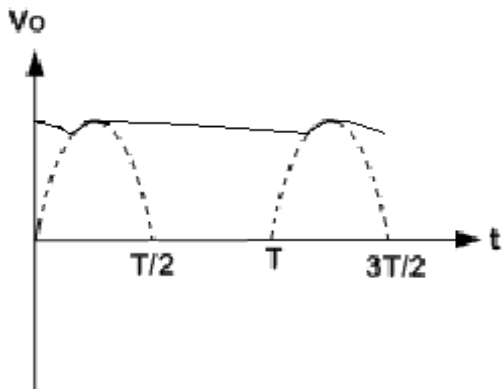

Peak output Voltage

$V_m =$ Ripple Factor =

$$\frac{V_{ac}}{V_{dc}} =$$

$$V_{dc} = \frac{V_m}{1 + \frac{1}{2fR_L C}} =$$

$$V_{ac} = \frac{V_{rp-p}}{2} =$$


$$V_{rms} = \sqrt{V_{dc}^2 + V_{ac}^2} =$$

$$\text{Rectifier efficiency } \eta_{\frac{P_{dc}}{P_{ac}}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$


$$\% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 =$$

II) Full wave Rectifier without

Filter: Circuit Diagram:

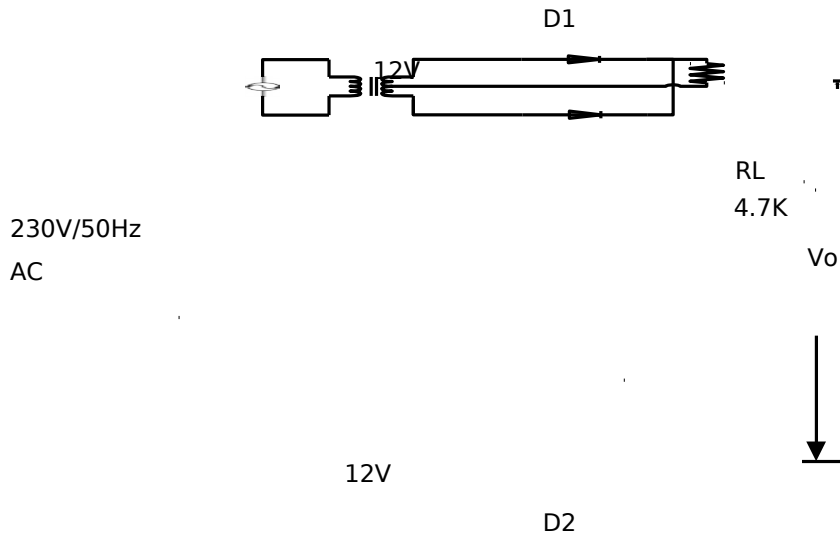

Waveforms:

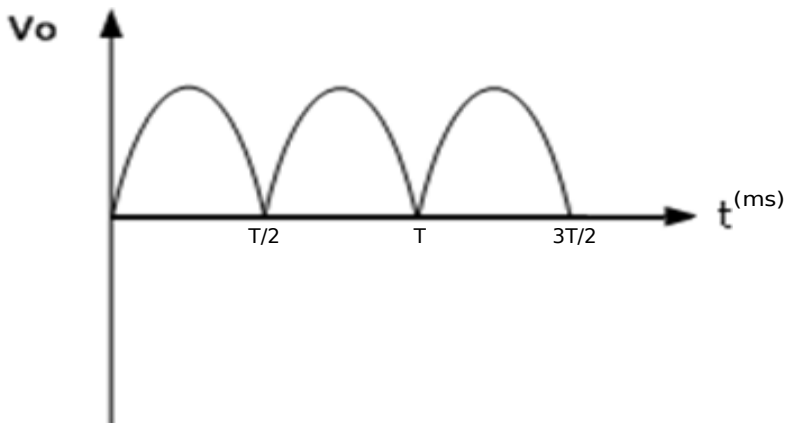

$$V_{dc} = \frac{2V_m}{\pi} =$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} =$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} =$$


$$\gamma = \frac{V_{ac}}{V_{dc}} =$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$


$$\% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 =$$

III) Full wave Rectifier with

Filter: Circuit Diagram:

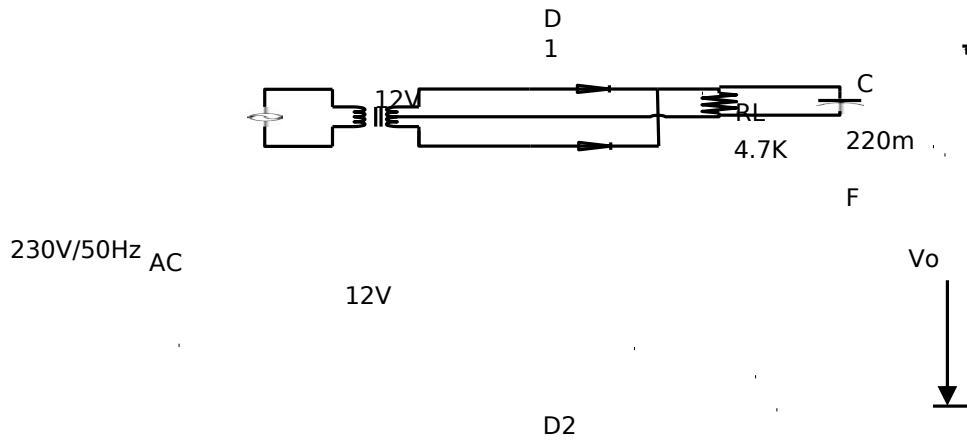

Waveforms:

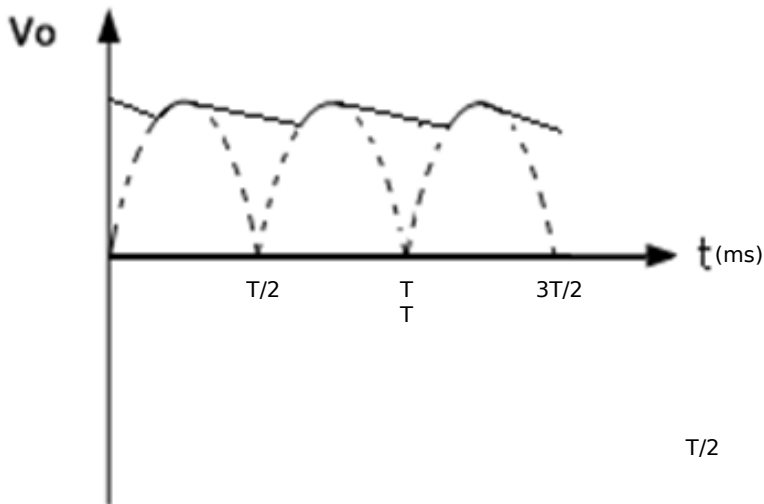


$$V_{dc} = \frac{V_m}{1 + \frac{1}{4fR_L C}} =$$

$$\gamma = \frac{V_{ac}}{V_{dc}}$$


$$V_{ac} = \frac{V_{r-(p-p)}}{2\sqrt{3}} = V_{rms} = \sqrt{V_{dc}^2 + V_{ac}^2} =$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$

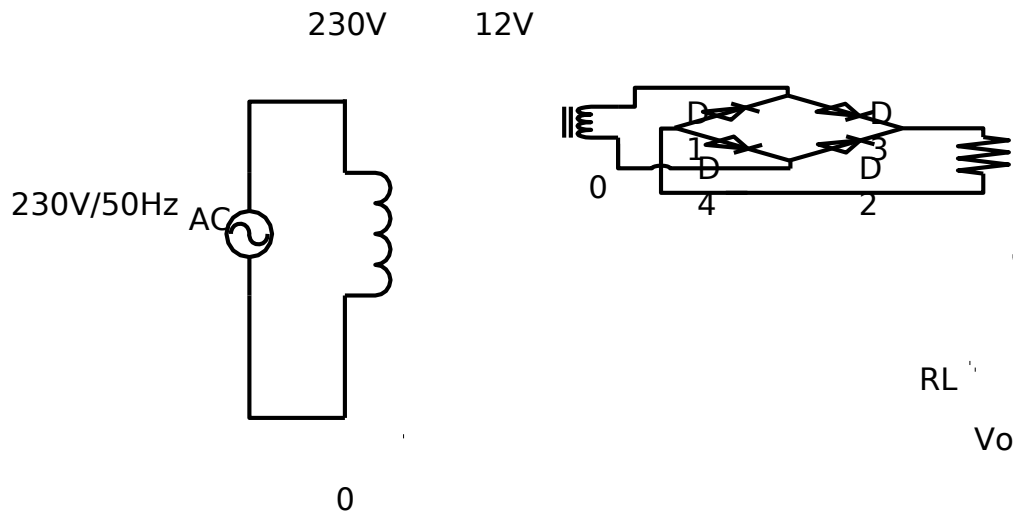Bridge Rectifier without Filter: Circuit Diagram:



Waveforms:

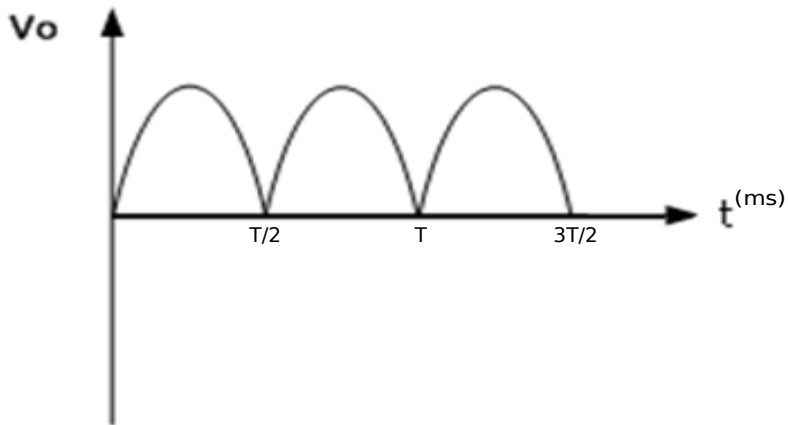

$$V_{dc} = \frac{2V_m}{\pi} =$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} =$$

$$V_{ac} = \sqrt{V_{rms}^2 - V_{dc}^2} =$$


$$\gamma = \frac{V_{ac}}{V_{dc}} =$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$


$$\% \text{ Regulation} = \frac{V_{dc(NL)} - V_{dc(FL)}}{V_{dc(FL)}} \times 100 =$$

Bridge Rectifier with

Filter: Circuit Diagram:

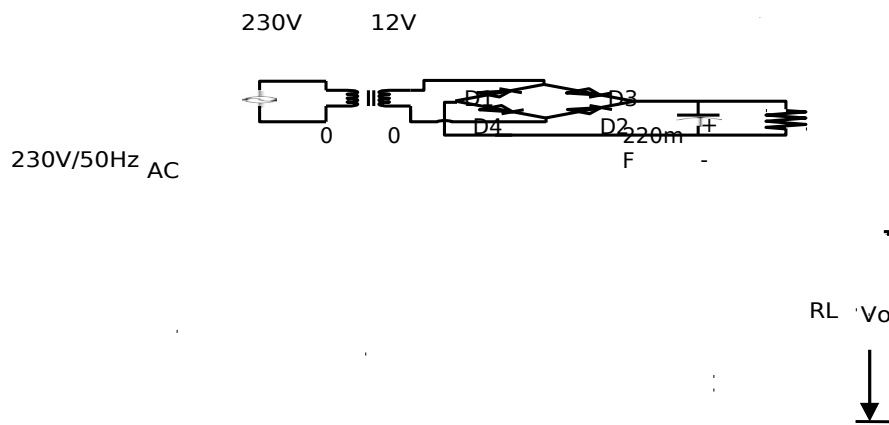

Waveforms:

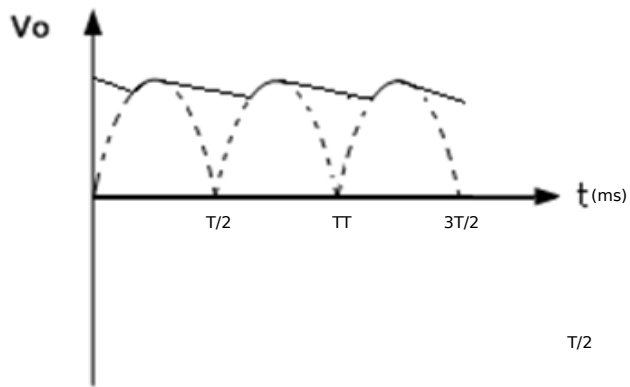

$$V_{dc} = \frac{V_m}{1 + \frac{1}{4fR_L C}} =$$

$$V_{ac} = \frac{V_{r-(p-p)}}{2\sqrt{3}} =$$

$$\gamma = \frac{V_{ac}}{V_{dc}} =$$

$$V_{rms} = \sqrt{V_{dc}^2 + V_{ac}^2} =$$

$$\eta = \frac{P_{dc}}{P_{ac}} = \left[\frac{V_{dc}}{V_{rms}} \right]^2 =$$

Procedure:

- Make the Connections as shown in the circuit diagram
- Apply 230V AC supply from the power mains to the primary of the transformer
- Observe the voltage across secondary to get V_m , the peak value in CRO
- Use relevant formula to find V_{dc} and V_{rms} of both Full wave and Half wave rectifier & draw the waveforms
- Find out the Ripple factor, Regulation and Efficiency by using the formula.

Conclusions:

R.C.PHASE SHIFT OSCILLATOR

Aim: To design and test the RC Phase shift Oscillator for the frequency of 1KHz.

Components required:

- Transistor (BC 107)
- Resistors
- CRO
- Capacitors

Desig**n:**

$$V_{CC} =$$

$$12V \quad I_C =$$

$$2mA$$

$$V_{RC} = 40\% \quad V_{CC} =$$

$$4.8V \quad V_{RE} = 10\%$$

$$V_{CC} = 1.2V \quad V_{CE} =$$

$$50\% \quad V_{CC} = 6V$$

To find R_C , R_1 , R_E & R_2

We Have,

$$V_{RC} =$$

$$I_C R_C = 4.8V \quad R_C$$

$$= 2.4K\Omega$$

$$\text{Choose } R_C = 2.2K\Omega$$

$$V_{RE} =$$

$$I_E R_E = 1.2V \quad R_E$$

$$= 600\Omega$$

$$\text{Choose } R_E = 680\Omega$$

$$h_{fe} = 100 \text{ (For BC}$$

$$107) I_B = \frac{I_C}{h_{fe}} =$$

20mA

Assume current through $R_1 = 10 I_B$ & through

$$R_2 = 9 I_B \quad V_{R_1} = V_{CC} - V_{R_2}$$

$$= 10V$$

$$\text{Also, } V_{R_1} = 10 I_B \quad R_1 = 10.1V$$

$$R_1 = 50\text{K}\Omega$$

Choose $R_1 = 47\text{K}\Omega$

$$V_{R_2} = V_{BE} + V_{RE}$$

$$= 0.7 + 1.2$$

$$= 1.9\text{V}$$

Also, $V_{R_2} = 9 I_B$

$$R_2 = 1.9\text{V} / I_B =$$

$$10.6\text{K}\Omega$$

Choose $R_1 = 12\text{K}\Omega$

To find C_C & C_E

$$X_{C_E} = \frac{1}{2\pi C_E} = \frac{1}{10} R_E = \frac{680}{10} = 68\Omega$$

For $\vartheta =$

$$20\text{Hz} \quad C_E =$$

$$117 \quad \mu\text{F}$$

Choose $C_E = 220\mu\text{F}$

$$X_{C_C} = \frac{1}{2\pi C_C} = \frac{R_C}{10} = 220\Omega$$

For $\vartheta = 20\text{Hz}$

$$\text{Choose } C_C =$$

$$47 \quad \mu\text{F}$$

Design of Selective Circuit:

Required ϑ of oscillations $f = 1\text{KHz}$

$$f = \frac{1}{2\pi R C \sqrt{6 + \frac{4R_C}{R}}}$$


Take $R = 4.7\text{K}\Omega$ & $C = 0.01\mu\text{F}$

Procedure:

- Rig up the circuit as shown in the figure
- Observe the sinusoidal output voltage.

- Measure the frequency and compare with the theoretical values.

Circuit Diagram:

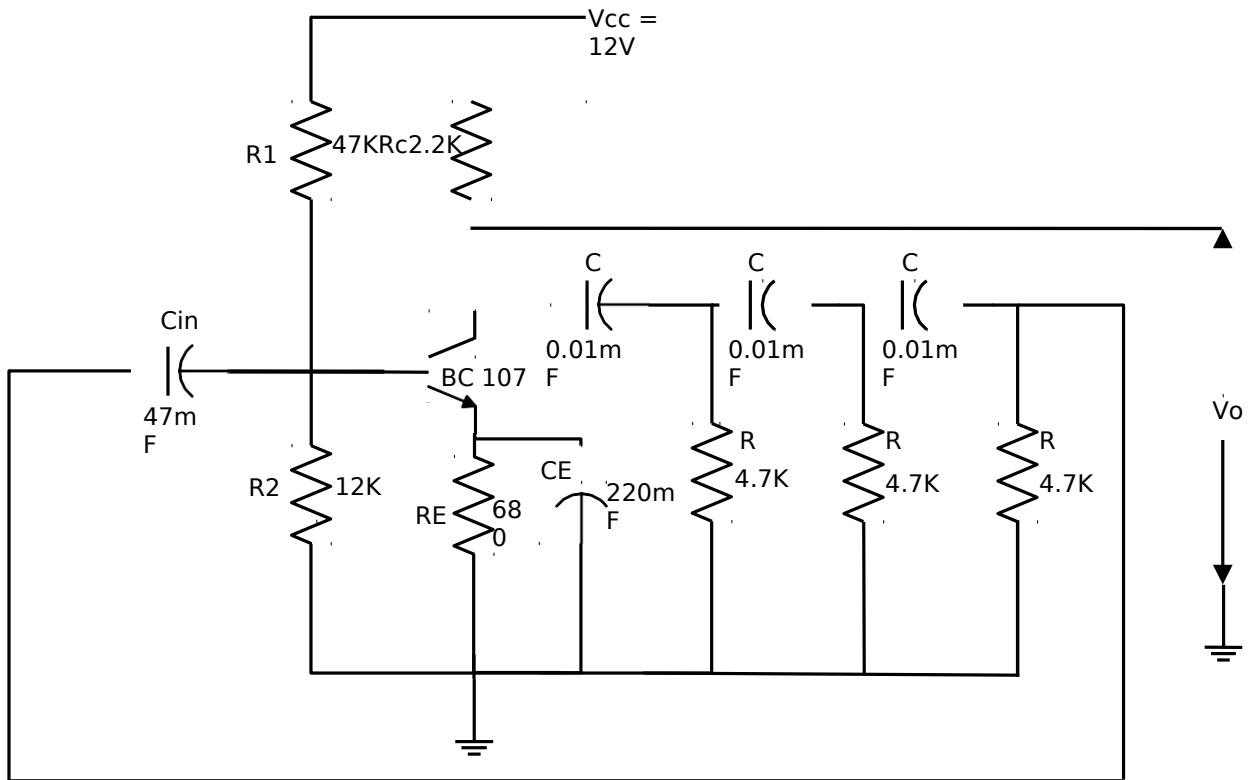

Result:

Frequency

Theoretical: 1KHz

Practical: _____


CLASS 'B' PUSH-PULL AMPLIFIER

Aim: To design and test the performance of transformer less Class 'B' Push-Pull Amplifier and to determine its conversion efficiency.

Components Required:

- Diodes IN 4001
- Transistor SL100, SK100
- Resistors
- Capacitors

Circuit Diagram:

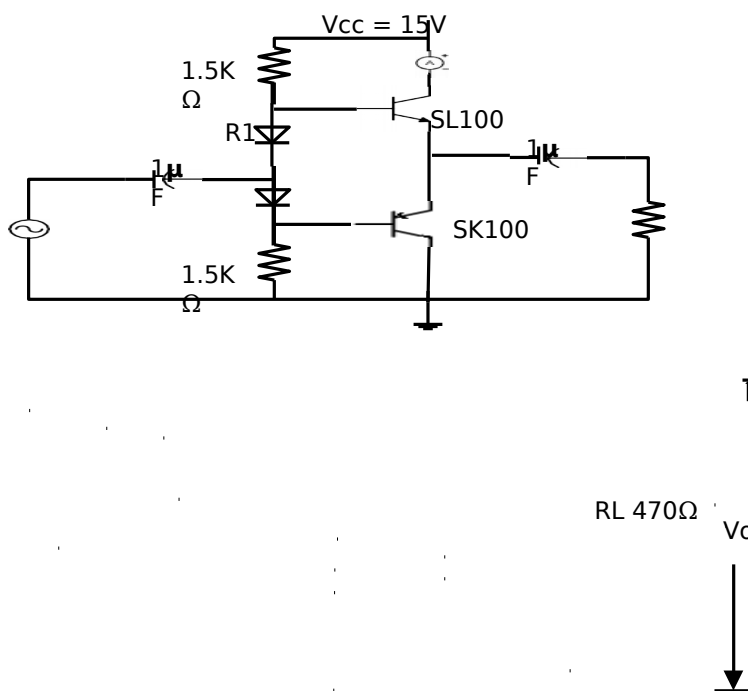

Design:

Given $V_{CC} = 15V$, $R_L = 470\Omega$

$$V_{CE1} = V_{CE2} = \frac{V_{CC}}{2} =$$

$$7.5V$$

$$V_{B1} = V_{CE2} + V_{BE1} = 7.5 + 0.7 = 8.2V$$

Assume $I_1 = 5mA$

R

₁
=

$$\frac{V_{CC}}{I_1}$$

=

1

·

3

6

K

Ω

R

₂
=

$$\frac{V_{R2}}{I_1}$$

=

$$\frac{V_{B1}}{I_1}$$

1

·

3

6

K

Ω

C

h

o

s

e

R

₁
=

R

₂
=

1

·

5

K

Ω

Choose $C_1 = C_2 = 1\mu\text{F}$

$$P_i(\text{dc}) = V_{CC} I_{dc}$$

$$P_o(\text{ac}) = \frac{V_m^2}{2R_L}$$

Efficiency $\eta =$

$$\frac{P_o(\text{ac})}{P_i(\text{dc})}$$

Procedure:

- Connect the circuit as shown in the circuit diagram.
- Apply the input voltage $V_i = 5\text{V}$
- Keeping the voltage constant, vary the frequency from 100Hz to 1MHz in regular steps and note down the output voltage in each case.
- Plot the gain Vs Frequency graph.
- Note down the dc current I_{dc}
- Calculate the efficiency.

Observations:

$$V_i = 5\text{V}$$

Freq. in Hz	V_o	Gain=	Gain in dB $= 20 \log \frac{V_o}{V_i}$
50 Hz			
100 Hz			
200 Hz			
500 Hz			
1 KHz			
2 KHz			
3 KHz			
5 KHz			
10 KHz			
.			
.			
.			

.			
1MHz			
2 MHz			

Result:

Efficiency $\eta =$

AIM: To check the following applications of OP-AMP.

- a) Inverting Amplifier. b) Non inverting amplifier.

APPARATUS:

S.No	Name	Range / Value	Quantity
1.	Fixed power supply	[- 15V - 0V - +15V]	1
2.	OP-AMP	μ A741C	1
3.	Resistors	1K Ω , 4.7K Ω , 10K Ω , 33K Ω	Each 1
4.	Function generator	--	1
5.	CRO	--	1


PROCEDURE:

INVERTING & NON - INVERTING AMPLIFIER:


1. Connect the circuit as shown in the figure -1
2. Switch on the power supply and signal generator.
3. Apply a sinusoidal signal with peak to peak amplitude of 20mV at a frequency of 1KHz.
4. Note down the amplitude of O/P signal in the C.R.O.
5. Repeat the above steps for different values of R_f .
6. Repeat the above steps for the circuit of fig -2.
7. Tabulate the readings.

CIRCUIT DIAGRAM:

Inverting Amplifier:

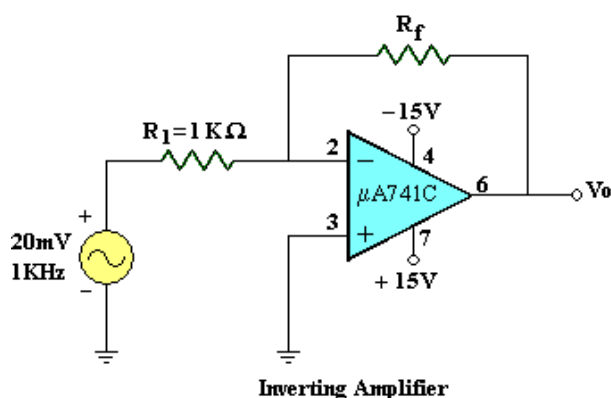

Non - inverting Amplifier:

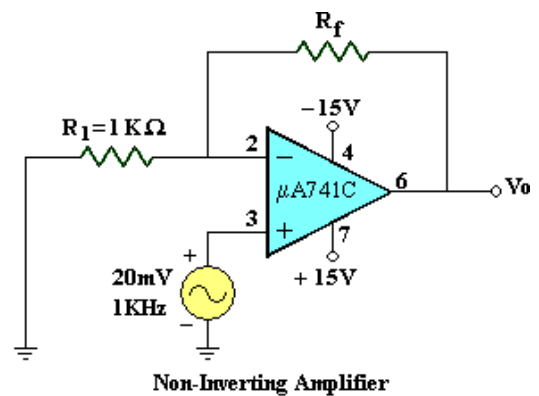

INVERTING AMPLIFIER:

$V_i = 20\text{mV}$

S.N O	R_f (Ω)	$R_1(\Omega)$	V_o (mV)	Gain = V_o / V_i	Theoretical Gain = ($-R_f/R_1$)
1	4.7K	1K			
2	10K	1K			
3	33K	1K			

NON-INVERTING AMPLIFIER:

$V_i = 20\text{mV}$

S.N O	R_f (Ω)	$R_1(\Omega)$	V_o (mV)	Gain = V_o / V_i	Theoretical Gain = ($1+R_f/R_1$)
1	4.7K	1K			
2	10K	1K			
3	33K	1K			

RESULT-

EXP-7

COLPITTS OSCILLATOR

AIM: To determine the frequency of oscillations of a given Colpitts Oscillator.

APPARATUS:


S.No	Name	Range / Value	Quantity
1.	DC Regulated Power Supply	(0-30V)	1
2.	Resistors	560 Ω , 47 K Ω	Each 1
4.	Resistors	4.7 K Ω	2
5.	Capacitors	100 μ F, 0.047 μ F	Each 1
6.	Decade Inductance Box	--	1
7.	Decade Capacitance Box	--	2
8.	CRO	--	1

PROCEDURE:

1. Connect the circuit diagram as shown in the figure.
2. Switch on the power supply.
3. Connect the out put terminals to CRO.
4. Adjust the capacitances until a sinusoidal wave form is observed on the CRO.
5. Measure the time period of the sinusoidal wave form (T) and determine the Frequency (1/T).
6. Repeat the above steps for different values of L, C₁ & C₂.

7. Tabulate the readings and compare with theoretical values

CIRCUIT DIAGRAM

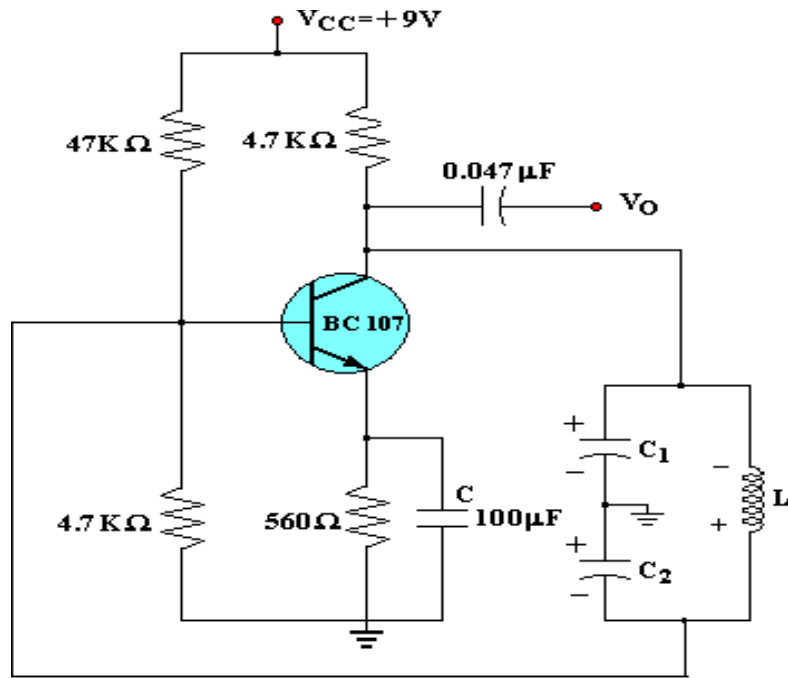

Colpitts Oscillator

TABULAR FORM:

S.NO	L (mH)	C (μF)		Practical frequency (Hz)	Theoretical Frequency (Hz)
		C ₁	C ₂		
1					
2					
3					

CALCULATIONS:

f_0 (practical) = $1/T$ Hz.

f_0 (theoretical) $f = \frac{1}{2\pi \sqrt{L \times \frac{C_1 C_2}{C_1 + C_2}}}$. [Where $\frac{C_1 C_2}{C_1 + C_2}$]

WEIN BRIDGE OSCILLATOR

AIM: To determine the frequency of oscillations of a given Wein Bridge oscillator and compare it with the theoretical value.


APPARATUS:

S.No	Name	Range / Value	Quantity
1.	Fixed Power Supply	[- 15V - 0V - +15V]	1
2.	OP-AMP	μ A741C	1
3.	Potentiometer	47 K Ω	1
4.	Resistors	3.3 K Ω , 220 Ω	Each 2
5.	Resistors	12 K Ω	1
6.	Capacitors	0.047 μ F, 0.33 μ F	Each 2
7.	CRO.	--	1

PROCEDURE:

1. Connect the circuit as shown in the figure.
2. Connect 0.047 μ F, and 3.3 K Ω in place of C and R.
3. Connect the O/P to the C.R.O and observe the sinusoidal signal and measure its frequency.
4. Connect 0.33 μ F, and 220 Ω in places of C and R.
5. Observe the sinusoidal signal and measure its frequency.
6. Tabulate the readings and Compare it with theoretical values

CIRCUIT DIAGRAM:

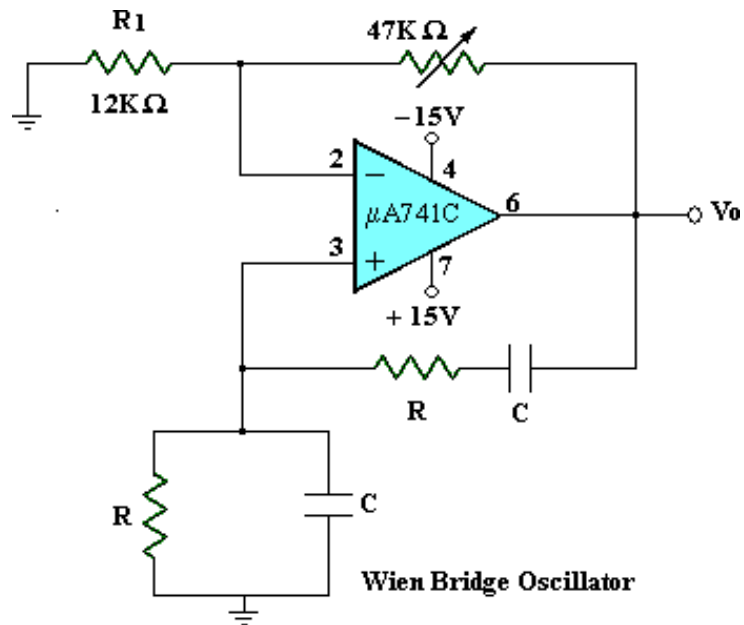

TABULAR FORM:

S.No	Capacitance C (μ F)	Resistance R (Ω)	Theoretical Frequency = $1/2\pi RC$ (Hz)	Practical Frequency = $1/T$ (Hz)
1	0.047	3.3 K		
2	0.33	220		

FORMULAS:

Practical Frequency = $f_o = 1/T$

Theoretical Frequency = $1/2\pi RC$

EXP-9

HARTLEY OSCILLATOR

AIM: To Determine the frequency of oscillations of a Hartley Oscillator and compare it with the theoretical values.

APPARATUS:


S.No	Name	Range / Value	Quantity
1.	D.C Regulated Power Supply	(0 - 30V)	1
2.	Resistors	1K Ω , 10k Ω , 47K Ω	Each 1
3.	Capacitors	0.22 μ F	2
4.	Decade Capacitance Box	--	1
5.	Decade Inductance Box	--	2
6.	CRO	--	1

--	--	--	--

PROCEDURE:

1. Connect the circuit as shown in the figure.
2. Connect the O / P of the oscillator to the C.R.O.
3. Adjust the Capacitance and Inductance Boxes until a sinusoidal signal is observed in the CRO.
4. Determine the frequency of the wave form.
5. Determine the frequency by varying the capacitance in convenient steps.
6. Tabulate the readings and compare the readings with the theoretical values.

CKT DIA.

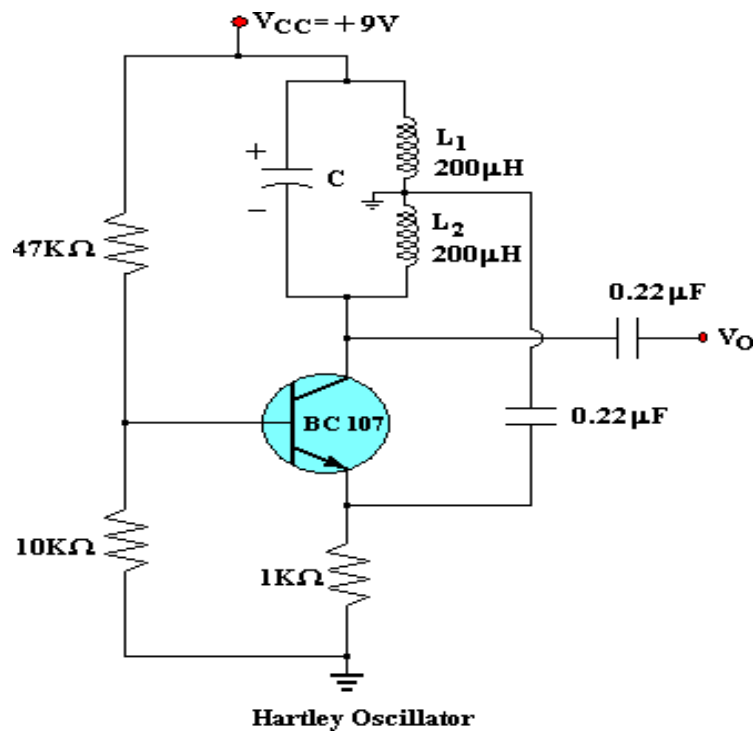

TABULAR FORM:

Capacitance C (μ F)	Inductance (m H)		Practical Frequency (Hz)	Theoretical Frequency (Hz)
	L ₁	L ₂		

--	--	--	--

FORMULAS:

Theoretical Frequency $f_0 = 1/2\pi\sqrt{LC}$

Practical Frequency $F = 1/T$